

2015

PHYSICS

( Major )

Paper : 5.4

( **Electronics** )

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks  
for the questions*

1. Answer the following questions very  
briefly : 1×7=7

- (a) How does the peak inverse voltage (PIV) for a half-wave rectifier change when a capacitor filter is used?
- (b) Which diode is also called the negative resistance semiconductor diode? Why is it so called?
- (c) Give the statement of Millman's theorem with its importance.

- (d) For a power amplifier using radio-frequency signal, what type of coupling is preferred?
- (e) Mention the type of feedback required to obtain undamped oscillations with reasons.
- (f) Explain the principle that modern radio receivers employ.
- (g) In what respects does the output voltage of a real OP-AMP differ from that of an ideal OP-AMP?

2. Answer the following questions : 2×4=8

- (a) What is the need of stabilization of Q-point of a transistor amplifier?
- (b) What changes are to be made to make a positive clamping circuit to a negative clamping circuit?
- (c) Draw the circuit diagram of an astable (free running) multivibrator.
- (d) A 741 is an OP-AMP with  $A = 30000$  and  $CMRR_{dB} = 9$  dB. What is the common-mode voltage gain?

( 3 )


3. A transistor having  $\alpha = 0.98$  has a reverse saturation current  $I_{CO} = 10 \mu\text{A}$  and is operated in CB configuration. If the base current is 3 mA, calculate the following : 5

- (a)  $\beta$  for transistor  
(b) Collector current  $I_C$   
(c) Emitter current  $I_E$

Or

Draw the circuit diagram of a full-wave rectifier feeding an inductor filter and a load resistance. Calculate the ripple factor for such a circuit. 5

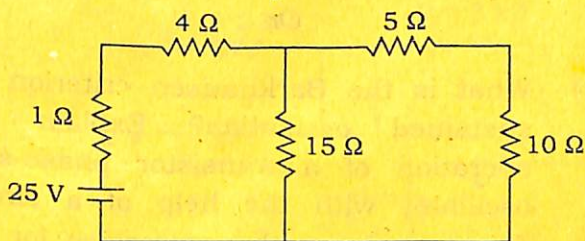4. Using Norton's theorem, find the current through resistance  $10 \Omega$  of the following circuit. Draw the equivalent circuit : 5



5. Draw the circuit diagram of a two-stage RC-coupled amplifier and calculate the voltage gain in the mid-frequency range. What is meant by frequency-response curve? 5

6. Answer either (a) and (b) or (c) and (d) of the following questions : 5+5=10

(a) What is a regulated power supply? Draw the circuit diagram of a series voltage regulator and explain its principle of operation.

(b) A CE amplifier has a load resistance of  $3 \text{ k}\Omega$  and an emitter load resistance  $R_E = 100 \Omega$ . The  $h$ -parameters are

$$h_{ie} = 4000 \Omega, h_{re} = 7 \times 10^{-4}, h_{fe} = 135$$

$$\text{and } h_{oe} = 25 \mu\text{A/V}$$

Determine the current gain, the input resistance, the output resistance and the voltage gain.

Or

(c) What is the Barkhausen criterion for sustained oscillation? Explain the operation of a transistor phase-shift oscillator with the help of a circuit diagram. Derive the expression for the frequency of oscillation.

(d) Show that negative feedback improves the stability of the gain and reduces the frequency distortion of an amplifier.

( 5 )

7. Answer either (a) and (b) or (c) and (d) of the following questions : 5+5=10


(a) (i) Convert binary 101.1101 to its decimal equivalent.

(ii) Convert decimal 1256.25 to its binary equivalent.

(iii) Add  $1101 + 101 + 10 + 1$ .

(iv) Subtract  $11000.11 - 101.111$  using 2's complement method.

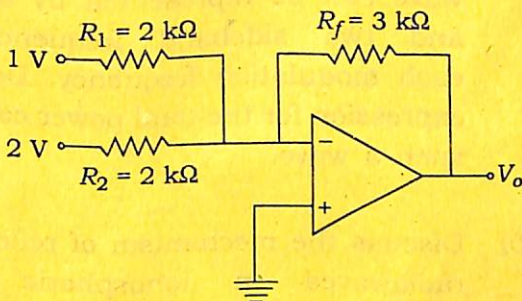(b) Calculate the output of an OP-AMP ( $V_o$ ) of the following circuit :



What is the output when  $R_1$  is replaced by a  $1\text{ k}\Omega$  resistor?

Or

- (c) State De Morgan's theorems. Explain how you can realise NAND and NOR gates using diodes and transistors.
- (d) Show the working of a master-slave  $J-K$  flip-flop with the help of a circuit diagram. State how the race-around condition can be avoided by using this flip-flop. How can you convert  $J-K$  flip-flop to  $D$  flip-flop?
8. Answer either (a) and (b) or (c) and (d) of the following questions : 5+5=10
- (a) Show that an amplitude-modulated wave can be represented by a carrier and two sideband frequencies for each modulation frequency. Derive an expression for the total power carried by such a wave.
- (b) Discuss the mechanism of reflection of radiowaves in ionospheric layers. Explain the terms 'skip distance', 'maximum usable frequency (MUF)' and 'fading' in sky wave communications.

( 7 )

Or

- (c) What is SSB transmission? Why is it preferred? Describe with a block diagram a method for generating single-sideband.
- (d) Draw the block diagram of a general purpose CRO and indicate its basic components. How can the phase difference between two a.c. voltages be measured by a CRO using Lissajous' figure?

\*\*\*